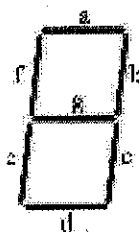


Draw the logic of one 7-segment display from binary coded decimal format (Conversion from 4 bit input [X,Y,Z,W] to 7 output bits [a,b,c,d,e,f,g] assuming each of the segment is illuminated upon 0 in output) using the given truth table. Write equations of Boolean Expressions and draw logic circuit over Logism, attach screenshot with this worksheet.



$$\begin{aligned} a &= \Sigma(0, 2, 3, 5, 7, 8, 9) \\ b &= \Sigma(0, 1, 2, 3, 4, 7, 8, 9) \\ c &= \Sigma(0, 1, 3, 4, 5, 6, 7, 8, 9) \\ d &= \Sigma(0, 2, 3, 5, 6, 8) \\ e &= \Sigma(0, 2, 6, 8) \\ f &= \Sigma(0, 4, 5, 6, 8, 9) \\ g &= \Sigma(2, 3, 4, 5, 6, 8, 9) \end{aligned}$$

$$\begin{aligned} a &= X + Z + YW + Y\bar{W} \\ b &= \bar{Y} + ZW + Z\bar{W} \\ c &= Y + \bar{Z} + W \\ d &= YW + Z\bar{W} + Y\bar{Z}W + \bar{Y}Z + X \\ e &= YW + Z\bar{W} \\ f &= X + Z\bar{W} + Y\bar{Z} + YW \\ g &= X + Y\bar{Z} + \bar{Y}Z + Z\bar{W} \end{aligned}$$

Truth Table:

| Digit | X | Y | Z | W | a | b | c | d | e | f | g |
|-------|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 2 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 4 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 6 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 7 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |

a)

| | $\bar{z}w$ | $\bar{z}\bar{w}$ | zw | $z\bar{w}$ |
|------------|------------|------------------|------|------------|
| $x\bar{y}$ | 1 | | 1 | 1 |
| $\bar{x}y$ | | 1 | 1 | 1 |
| xy | x | x | x | x |
| $x\bar{y}$ | 1 | 1 | x | x |

$x + z + yw + \bar{y}w$

b)

| | $\bar{z}w$ | $\bar{z}\bar{w}$ | zw | $z\bar{w}$ |
|------------|------------|------------------|------|------------|
| $x\bar{y}$ | 1 | | 1 | 1 |
| $\bar{x}y$ | 1 | | 1 | |
| xy | x | x | x | x |
| $x\bar{y}$ | 1 | 1 | x | x |

$\bar{y} + \bar{z}w + zw$

c)

| | $\bar{z}w$ | $\bar{z}\bar{w}$ | zw | $z\bar{w}$ |
|------------|------------|------------------|------|------------|
| $x\bar{y}$ | 1 | 1 | 1 | |
| $\bar{x}y$ | 1 | 1 | 1 | 1 |
| xy | x | x | x | x |
| $x\bar{y}$ | 1 | 1 | x | x |

$y + \bar{z} + w$

d)

| | $\bar{z}w$ | $\bar{z}\bar{w}$ | zw | $z\bar{w}$ |
|------------|------------|------------------|------|------------|
| $x\bar{y}$ | 1 | | 1 | 1 |
| $\bar{x}y$ | | 1 | | 1 |
| xy | x | x | x | x |
| $x\bar{y}$ | 1 | 1 | x | x |

$\bar{y}w + z\bar{w} + y\bar{z}w + \bar{y}z + x$

e)

| | $\bar{z}w$ | $\bar{z}\bar{w}$ | zw | $z\bar{w}$ |
|------------|------------|------------------|------|------------|
| $x\bar{y}$ | 1 | | | 1 |
| $\bar{x}y$ | | | | 1 |
| xy | x | x | x | x |
| $x\bar{y}$ | 1 | | x | x |

$\bar{y}w + z\bar{w}$

f)

| | $\bar{z}w$ | $\bar{z}\bar{w}$ | zw | $z\bar{w}$ |
|------------|------------|------------------|------|------------|
| $x\bar{y}$ | 1 | | | |
| $\bar{x}y$ | 1 | 1 | | 1 |
| xy | x | x | x | x |
| $x\bar{y}$ | 1 | 1 | x | x |

$x + \bar{z}w + y\bar{z} + y\bar{w}$

g)

| | $\bar{z}w$ | $\bar{z}\bar{w}$ | zw | $z\bar{w}$ |
|------------|------------|------------------|------|------------|
| $x\bar{y}$ | | | 1 | 1 |
| $\bar{x}y$ | 1 | 1 | | 1 |
| xy | x | x | x | x |
| $x\bar{y}$ | 1 | 1 | x | x |

$x + y\bar{z} + \bar{y}z + z\bar{w}$