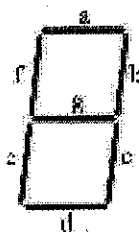


Draw the logic of one 7-segment display from binary coded decimal format (Conversion from 4 bit input [X,Y,Z,W] to 7 output bits [a,b,c,d,e,f,g] assuming each of the segment is illuminated upon 0 in output) using the given truth table. Write equations of Boolean Expressions and draw logic circuit over Logism, attach screenshot with this worksheet.



$$\begin{aligned} a &= \Sigma(0, 2, 3, 5, 7, 8, 9) \\ b &= \Sigma(0, 1, 2, 3, 4, 7, 8, 9) \\ c &= \Sigma(0, 1, 3, 4, 5, 6, 7, 8, 9) \\ d &= \Sigma(0, 2, 3, 5, 6, 8) \\ e &= \Sigma(0, 2, 6, 8) \\ f &= \Sigma(0, 4, 5, 6, 8, 9) \\ g &= \Sigma(2, 3, 4, 5, 6, 8, 9) \end{aligned}$$

$$\begin{aligned} a &= X + Z + YW + Y\bar{W} \\ b &= \bar{Y} + ZW + Z\bar{W} \\ c &= Y + \bar{Z} + W \\ d &= YW + Z\bar{W} + Y\bar{Z}W + \bar{Y}Z + X \\ e &= YW + Z\bar{W} \\ f &= X + Z\bar{W} + Y\bar{Z} + YW \\ g &= X + Y\bar{Z} + \bar{Y}Z + Z\bar{W} \end{aligned}$$

Truth Table:

Digit	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0

a)

	$\bar{z}w$	$\bar{z}\bar{w}$	$zw$	$z\bar{w}$
$x\bar{y}$	1		1	1
$\bar{x}y$		1	1	1
$xy$	x	x	x	x
$x\bar{y}$	1	1	x	x

$x + z + yw + \bar{y}w$

b)

	$\bar{z}w$	$\bar{z}\bar{w}$	$zw$	$z\bar{w}$
$x\bar{y}$	1		1	1
$\bar{x}y$	1		1	
$xy$	x	x	x	x
$x\bar{y}$	1	1	x	x

$\bar{y} + \bar{z}w + zw$

c)

	$\bar{z}w$	$\bar{z}\bar{w}$	$zw$	$z\bar{w}$
$x\bar{y}$	1	1	1	
$\bar{x}y$	1	1	1	1
$xy$	x	x	x	x
$x\bar{y}$	1	1	x	x

$y + \bar{z} + w$

d)

	$\bar{z}w$	$\bar{z}\bar{w}$	$zw$	$z\bar{w}$
$x\bar{y}$	1		1	1
$\bar{x}y$		1		1
$xy$	x	x	x	x
$x\bar{y}$	1	1	x	x

$\bar{y}w + z\bar{w} + y\bar{z}w + \bar{y}z + x$

e)

	$\bar{z}w$	$\bar{z}\bar{w}$	$zw$	$z\bar{w}$
$x\bar{y}$	1			1
$\bar{x}y$				1
$xy$	x	x	x	x
$x\bar{y}$	1		x	x

$\bar{y}w + z\bar{w}$

f)

	$\bar{z}w$	$\bar{z}\bar{w}$	$zw$	$z\bar{w}$
$x\bar{y}$	1			
$\bar{x}y$	1	1		1
$xy$	x	x	x	x
$x\bar{y}$	1	1	x	x

$x + \bar{z}w + y\bar{z} + y\bar{w}$

g)

	$\bar{z}w$	$\bar{z}\bar{w}$	$zw$	$z\bar{w}$
$x\bar{y}$			1	1
$\bar{x}y$	1	1		1
$xy$	x	x	x	x
$x\bar{y}$	1	1	x	x

$x + y\bar{z} + \bar{y}z + z\bar{w}$